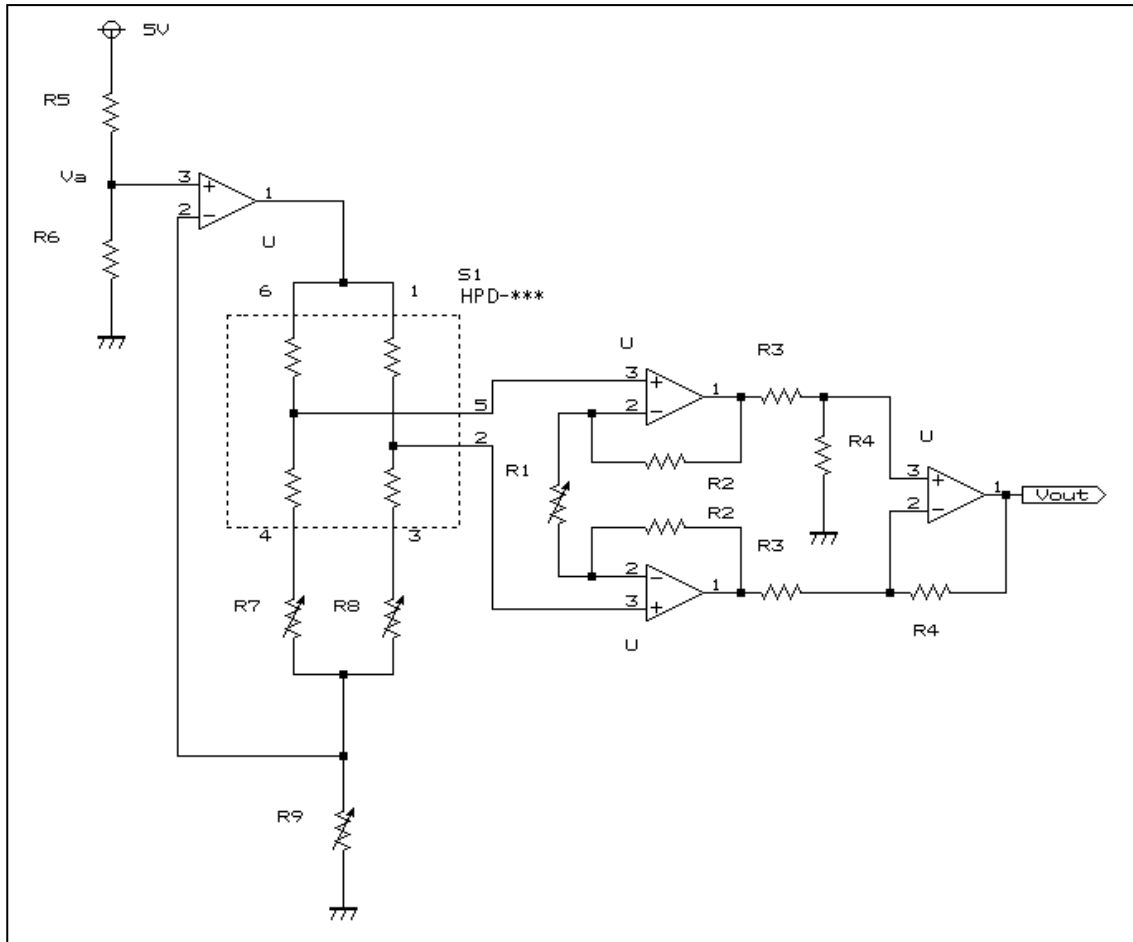


## Application circuit example



### ■ Amplifier circuit

The output voltage of the pressure sensor (HPD series) is about 1mV / kPa, which is a very small voltage when measuring a small pressure.

Therefore, it is recommended to use a differential amplifier circuit as described above to amplify the output in order to ensure reliable circuit operation.

For your reference, the post-amplification output calculation formula for this circuit is shown below.

$$V_{out} = V_{in} \cdot \frac{2R_2 + R_1}{R_1} \cdot \frac{R_4}{R_3}$$

The gain can be adjusted with R1 (or R3).

Vout is the output value after amplification, and Vin is the output value of the sensor element.

#### Constant current drive

It is recommended that the sensor be driven at a constant current of 1.5mA.

The setting can be adjusted with R9.

$$I_{drv} = V_a / R_9$$

#### Offset adjustment

It is recommended to adjust the offset voltage at 0 kPa.

The adjustment can be adjusted with R7 or R8.

Note: The sensor output should be received with high impedance.